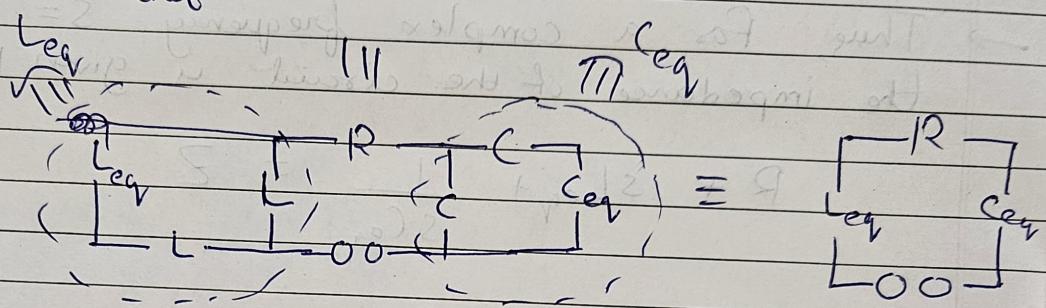


Repeating  
unit



Now

$$(i) \frac{1}{L_{eq}} + \frac{1}{L} = \frac{1}{L} + \frac{1}{L + L_{eq}}$$

$$\Rightarrow L_{eq} = \frac{L^2 + L \cdot L_{eq}}{2L + L_{eq}}$$

$$\Rightarrow L_{eq}^2 + L \cdot L_{eq} - L^2 = 0$$

$$\begin{aligned} \text{Solving, } L_{eq} &= -\frac{L \pm \sqrt{L^2 + 4L^2}}{2} \\ &= -L \pm \frac{\sqrt{5}L}{2} \end{aligned}$$

Discarding negative sol<sup>n</sup>  $| L_{eq} = \frac{\sqrt{5}-1}{2} L |$

$$(ii) C_{eq} = C + \frac{C \cdot C_{eq}}{C + C_{eq}}$$

$$\Rightarrow C_{eq}^2 - C^2 = C \cdot C_{eq}$$

$$\Rightarrow C_{eq}^2 - C \cdot C_{eq} - C^2 = 0$$

Solving,

$$C_{eq} = \frac{C \pm \sqrt{C^2 + 4L^2}}{2} = \frac{C \pm \sqrt{5}C}{2}$$

Discarding negative soln,  $C_{eq} = \left(\frac{\sqrt{5}+1}{2}\right) C$

→ Thus, for a complex frequency  $s = \sigma + j\omega$   
the impedance of the circuit is given by

$$R + sL_{eq} + \frac{1}{sC_{eq}} = Z$$

Resonance pole  $\Rightarrow Z = 0$

$$\Rightarrow s^2 L_{eq} C_{eq} + s R C_{eq} + 1 = 0$$

Solving for 's': we get

$$s = -\frac{R C_{eq}}{2 L_{eq} C_{eq}} \pm \sqrt{\frac{R^2 C_{eq}^2}{4 L_{eq} C_{eq}} - 1}$$

Now poles 's' depend on the value of  
discriminant  $\Delta = R^2 C_{eq}^2 - 4 L_{eq} C_{eq}$

(i)  $\Delta = 0$

$$\Rightarrow \sigma = s = \left| -\frac{R}{2 L_{eq}} \right| \Rightarrow \text{One real pole} \\ (\omega = 0)$$

(ii)  $\Delta > 0 \Rightarrow$

$$\left| \sigma = s = -\frac{R C_{eq}}{2 L_{eq} C_{eq}} \pm \sqrt{\Delta} \right| \Rightarrow \text{Two real poles} \\ (\omega = 0)$$

(iii)  $D < 0$

$$\Rightarrow s = \frac{-R C_{eq} \pm j \sqrt{4 L_{eq} C_{eq} - R^2 C_{eq}^2}}{2 L_{eq} C_{eq}}$$

$$\Rightarrow \sigma = \frac{-R}{2 L_{eq}}$$

$$\omega = \sqrt{\frac{1}{L_{eq} C_{eq}} - \left(\frac{R}{2 L_{eq}}\right)^2}$$